

Electronics Workshop 2 - 2026

Course Project 2

Team - Table 10 Lab Nilgiri 114

- **Name:** Ahamed Adikool Nishan
Roll Number: 2024112025
- **Name:** Bejaine Birju
Roll Number: 2024102060

Create a MEMS microphone preamplifier with automatic gain control (AGC) and anti-aliasing filter for always-on voice wake-word detection in smart home devices.

Proposed Solution

A low power circuit using a preamplifier circuit along with the MEMS microphone interface, succeeded by an automatic gain control (AGC) stage, a gain circuit, an Anti Aliasing Filter and an Active Band Pass Filter, connected to an ADC and the ESP, interfaced with a Language Model aboard a Raspberry Pi 4 for **wake word identification** and **querying**.

Stages

- Stage 1: MEMS Interface
- Stage 2: Pre-Amp Stage
- Stage 3: Automatic Gain Control
- Stage 4: Gain Stage
- Stage 5: Anti-Aliasing Filter
- Stage 6: Active Band Pass Filter
- Stage 7: ADC
- Stage 8: ESP32
- Stage 9: Raspberry Pi & TinyML model

Stage 1: MEMS Interface

Component: SPW2430 MEMS Microphone & Breakout Board

- Detects acoustic pressure and converts it to an analog voltage signal
- Small form factor, high sensitivity – ideal for voice recognition
- Requires 3.3V DC at V_{in} ; AC-coupled output fed to Pre-Amp
- Typical maximum output: $\approx 100 \text{ mV}_{pp}$

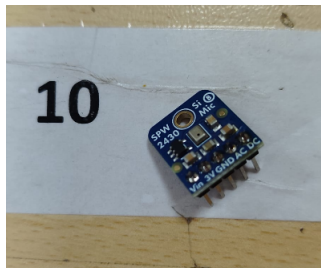


Figure: SPW2430 MEMS Microphone Module

Stage 2: Pre-Amplifier – Theory

Topology: Common-Emitter Differential Amplifier (NPN BJT pair)

- High input impedance, low output impedance, good noise rejection
- Amplifies differential signal; rejects common-mode noise (CMRR)
- **Single Input, Unbalanced Output** configuration used

Key gain expressions:

$$A_d = -\frac{g_m R_C}{2}, \quad A_c = -\frac{\alpha R_C}{r_e + 2R_{EE}}$$

$$\text{CMRR} = 20 \log \left(\frac{A_d}{A_c} \right) \approx 20 \log(g_m R_{EE})$$

Design target: Single-ended differential gain $A_d \approx 10$

Stage 2: Pre-Amplifier – Design

Component values:

- $R_C = 1.5\text{ k}\Omega$ (collector load)
- $R_{EE} = 3.3\text{ k}\Omega$ (tail resistor, -5 V rail)
- BJT: BC547B ($\beta = 200$)

Operating point:

$$I_C \approx 0.65\text{ mA}, \quad g_m \approx 26\text{ mA/V}$$

$$A_d \approx 19.5, \quad A_c \approx 0.23$$

$$\text{CMRR} \approx 38.7\text{ dB}$$

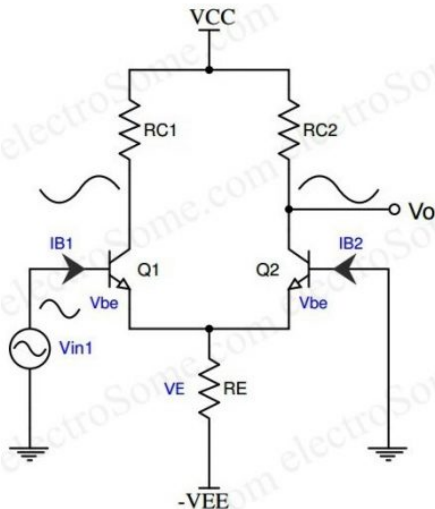


Figure: Pre-Amp Circuit Diagram

Stage 3: Automatic Gain Control (AGC)

Components:

- BF245B N-Channel JFET – Variable gain element
- UA741 Op-Amp – Inverting amplifier
- BC557C PNP BJT – Envelope detector
- $R_4 = 100\text{ k}\Omega$, $R_{17} = 10\text{ k}\Omega$, $C_2 = 10\text{ }\mu\text{F}$, $R_5 = 156\text{ k}\Omega$

Three functional blocks:

- 1 **Variable Gain Amplifier** – JFET as gate-controlled resistor
- 2 **Envelope Detector** – BC557C tracks signal peak into C_2
- 3 **Control Feedback** – V_C drives JFET gate (negative feedback)

AGC Theory: Variable Gain & Feedback

JFET channel resistance (ohmic region):

$$r_{DS}(V_{GS}) = \frac{r_{DS0}}{1 - V_{GS}/V_P}, \quad r_{DS0} = 250 \, \Omega, \quad V_P \approx -2 \, \text{V}$$

Inverting amplifier gain:

$$A_v(V_{GS}) = -\frac{R_4}{R_{17} + r_{DS}(V_{GS})} = -\frac{100 \, \text{k}}{10 \, \text{k} + r_{DS}}$$

Range: 0 to ≈ -9.76 (0 to ≈ 19.8 dB)


AGC time constants:

$$\tau_{\text{attack}} \ll 1 \, \text{ms}, \quad \tau_{\text{release}} = R_5 \cdot C_2 = 156 \, \text{k}\Omega \times 10 \, \mu\text{F} = \mathbf{1.56 \, \text{s}}$$

Slow release prevents “pumping” artefacts during speech pauses.

Output coupling: $f_c = 1/(2\pi \cdot 4.7 \, \text{k} \cdot 1 \, \mu) \approx 33.9 \, \text{Hz}$

AGC LTspice Simulation Circuit

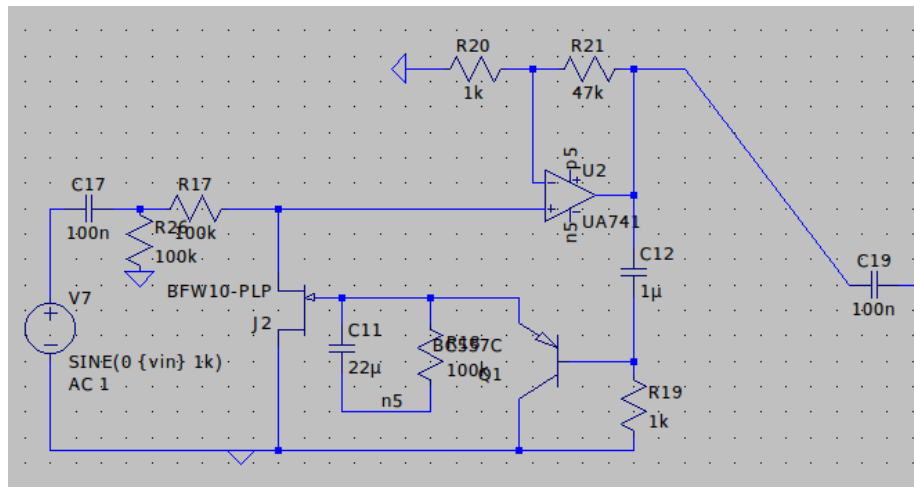

Stage 4: Gain Stage – Theory & Design

Topology: Common-Emitter amplifier with voltage-divider bias and split emitter resistors along with emitter degeneration.

We have designed for a voltage gain of 2.

The voltage gain]

Stage 5: Anti-Aliasing Filter (AAF) – Theory

Purpose: Low-pass filter before ADC to prevent aliasing (Nyquist–Shannon theorem)

Topology: 4th-order Butterworth – two cascaded 2nd-order Sallen-Key stages


- Maximally flat passband – minimal distortion over voice band
- Rolloff: -80 dB/decade beyond cutoff
- Cutoff set to 10 kHz (half the 20 kHz sampling rate)

Sallen-Key transfer function:


$$H(s) = \frac{1}{s^2 R_1 R_2 C_1 C_2 + s C_2 (R_1 + R_2) + 1}$$

$$\omega_c = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{C_2 (R_1 + R_2)}$$

AAF LTspice Simulation Circuit

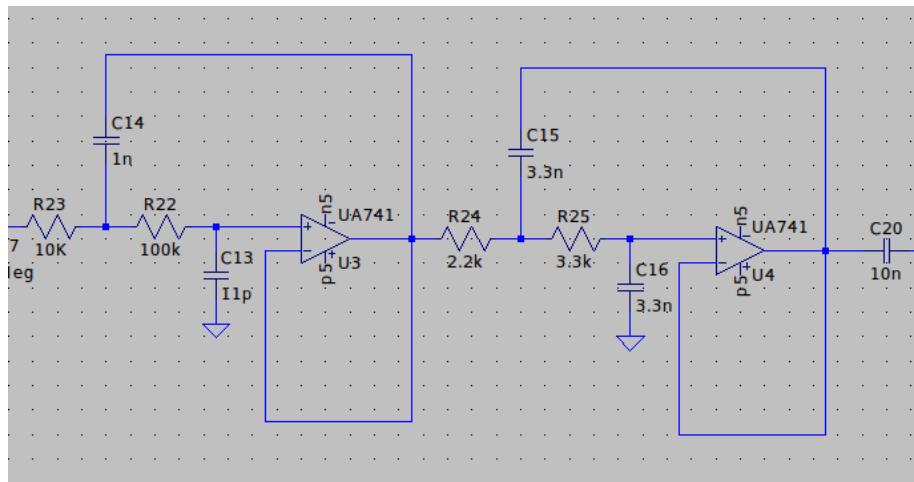

AAF Hardware Circuit

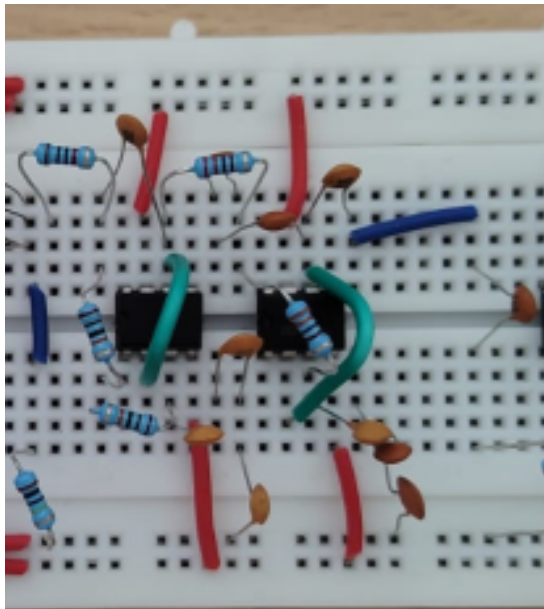

Stage 6: Active Band Pass Filter – Theory

Purpose: Provide high-pass filtering (DC blocking) and additional low-pass filtering with amplification in a single stage.

Topology: Passive HPF → Non-inverting Op-Amp → Passive LPF

Overall transfer function:

$$H(s) = \left(1 + \frac{R_4}{R_3}\right) \cdot \frac{sR_1 C_1}{(1 + sR_1 C_1)(1 + sR_2 C_2)}$$

Designed cutoffs:


$$f_{HP} = \frac{1}{2\pi \cdot 56 \text{ k} \cdot 47 \text{ n}} \approx 60.5 \text{ Hz}$$

$$f_{LP} = \frac{1}{2\pi \cdot 10 \text{ k} \cdot 2 \text{ n}} \approx 7.96 \text{ kHz}$$

Amplifier gain:

$$A_v = 1 + \frac{10 \text{ k}}{10 \text{ k}} = 2$$

BPF LTspice Simulation Circuit

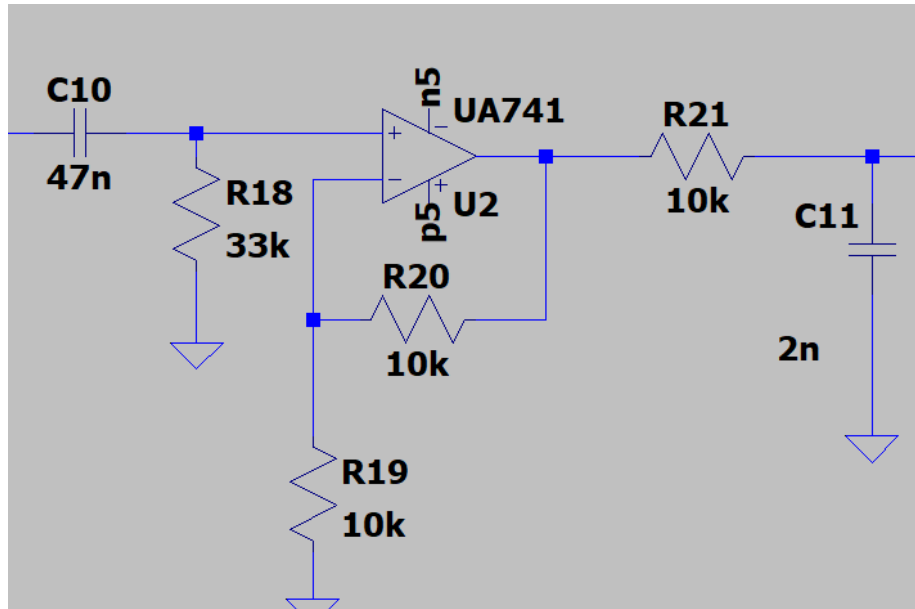

Input Protection: Schottky Diode Clamp (BAT54S)

Purpose: Protect ESP32 ADC from voltages outside 0–3.3 V

Topology: Rail-to-rail clamp ($V_F \approx 0.25\text{ V}$ for BAT54S)

$$V_{high} = 3.3 + 0.25 = \mathbf{3.55\text{ V}}, \quad V_{low} = 0 - 0.25 = \mathbf{-0.25\text{ V}}$$


Both within the ESP32 absolute maximum of 3.6 V.

In normal operation both diodes are reverse-biased and do not affect the signal. A standard silicon diode ($V_F \approx 0.65\text{ V}$) would clamp at 3.95 V – above the limit.

Stage 7: Analog-to-Digital Converter (PCM1808)

Component: PCM1808 Stereo ADC (Texas Instruments)

- Single-ended analog input, supports sample rates up to 96 kHz
- Operates in **slave mode** – I²S master clock provided by ESP32
- System clock: $256f_S$, $384f_S$, or $512f_S$ (auto-detected)
- 24-bit audio data, left-justified within 32-bit I²S frame

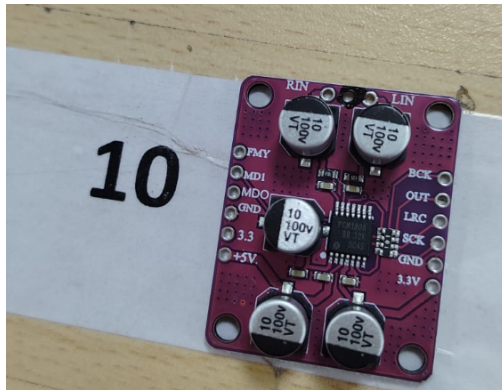

Stage 8: ESP32 – I²S Master & Serial Bridge

Role: Drive the PCM1808 ADC and stream audio to Raspberry Pi over UART

- I²S configured at **16 kHz**, 32-bit samples, mono (right channel)
- APLL enabled for low-jitter master clock on GPIO 3 (MCLK)
- BCK / LRCK / DATA on GPIOs 26 / 25 / 22
- Each 32-bit sample right-shifted by 16 bits → 16-bit PCM
- **Framed UART transmission at 460800 baud:**
 - 4-byte sync header: 0xDE 0xAD 0xBE 0xEF
 - 256 bytes audio payload (128 samples × 2 bytes)
- 8 DMA buffers × 512 bytes to prevent data loss

Stage 9: Raspberry Pi 4 – Wake Word Detection

Role: Host processor running the full wake-word pipeline

- ❶ **Frame Sync:** Scan byte stream for 0xDE 0xAD 0xBE 0xEF header
- ❷ **DSP Chain:**
 - 4th-order Butterworth BPF: 80–7500 Hz (SOS, 64-bit float)
 - Linear gain $5\times$, hard-clipped to 16-bit range
- ❸ **Wake-Word Inference:**
 - *openWakeWord* engine, pre-trained *Alexa* model
 - Input: 1280 samples (80 ms at 16 kHz)
 - Detection threshold: 0.1; debounce: 1.5 s

Final circuit demonstrated wake word detection with decent confidence scores in both noisy and non-noisy environments.

Echo Dot (3rd Generation) Power Consumption

Mode	Power Consumption (in Watts)
Off Mode* (Low Power Mode)	0.16
Networked Standby** (Automatic Sleep Mode, Microphones ON)	1.40
Networked Standby (Automatic Sleep Mode, Microphones OFF)	2.04

Figure: Power consumption metrics of the Amazon Alexa/Echo model with voice wake word detection [Click here](#)

Our Alexa!

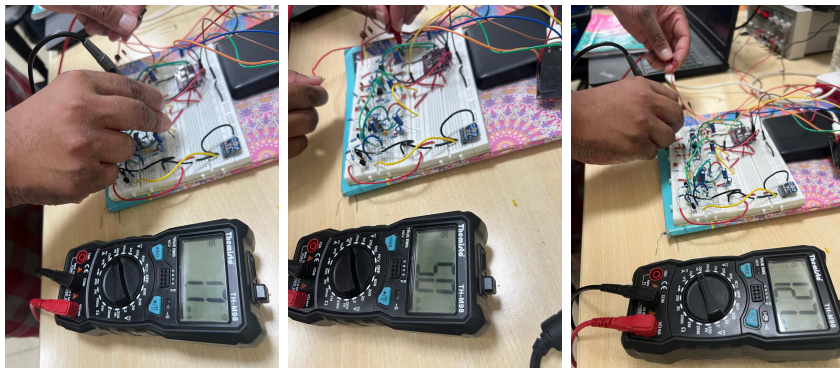


Figure: Pictures taken while measuring power consumed by our circuit

$$P_{\text{total}} = (3.3 \text{ V} \times 1.7 \text{ mA}) + (5 \text{ V} \times 12.7 \text{ mA}) + (5 \text{ V} \times 5 \text{ mA})$$

$$P_{\text{total}} = 5.61 \text{ mW} + 63.5 \text{ mW} + 25 \text{ mW} = \mathbf{94.11 \text{ mW}}$$

Conclusion

- Successfully designed and implemented a complete analog front-end for always-on wake word detection
- **Signal chain:** MEMS mic → Pre-Amp → AGC → Gain → AAF → BPF → ADC → ESP32 → Raspberry Pi
- AGC maintains constant output across varying speaker distances
- 4th-order Butterworth AAF provides -80 dB/decade attenuation
- **Total power consumption: 94.11 mW** (comparable to commercial devices)
- Wake word “Alexa” detected with good confidence in noisy and quiet environments